




Logical Design


CS 221

Prof.Dr. Mohamed Osama Khozium



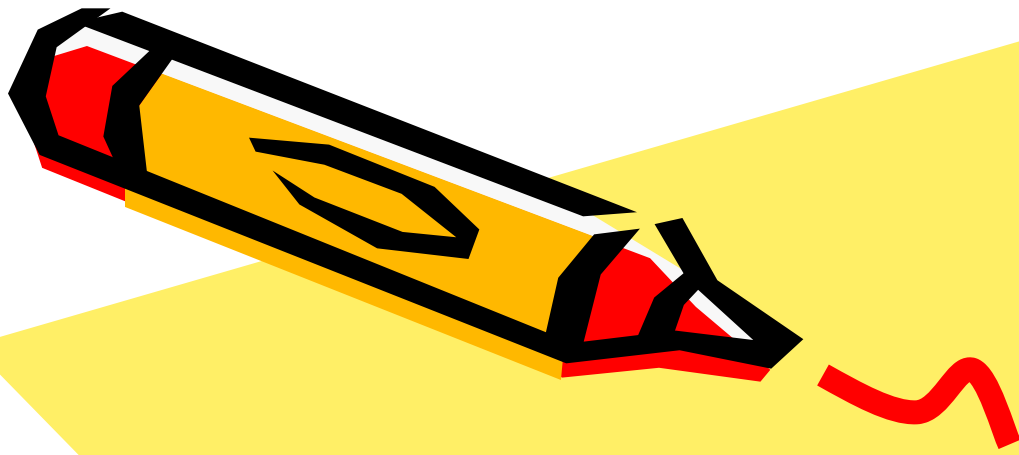

Simple Logic Gates & Boolean algebra

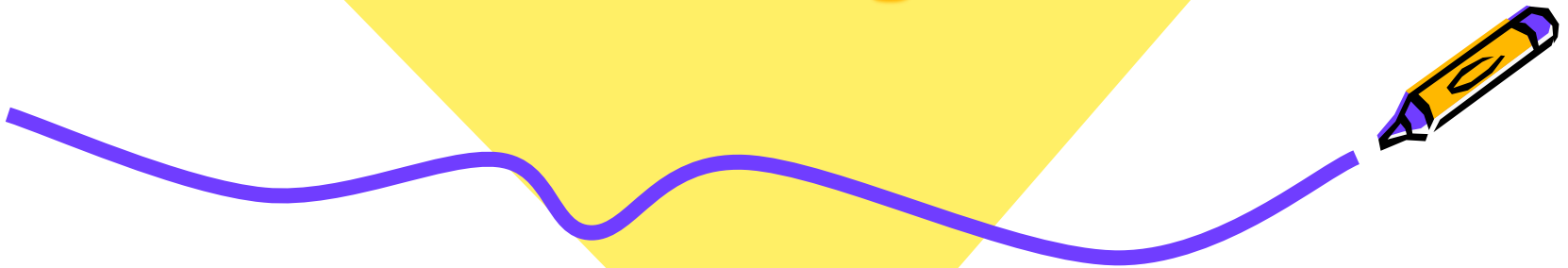



Module Outline



- Binary Logic and Basic Gates
- Boolean Algebra
- The Boolean expression for a logic circuit
- Implementation of a logic circuit using B.E
- Implementation of a logic circuit via truth table
- Converting a Boolean expression to a truth table
- Simplification of Boolean Functions





Binary Logic



- Deals with variables that take on only two discrete values and operations of mathematical logic that are applied to these variables
- The two values are known by different names:
 - HIGH and LOW
 - TRUE and FALSE
 - 0 and 1
- Variables may be denoted by any name but single letter character names such as *A*, *B*, *C*, *X*, *Y*, *Z*, etc. are common and easy to use





Logical Operations




- AND
 - Represented by a dot \cdot or sometimes \wedge or \cap
 - Binary operator, i.e. operates on two variables at a time
- OR
 - Represented by a $+$ or sometimes \vee or \cup
 - Binary operator, i.e. operates on two variables at a time
- NOT
 - Represented by a bar over the variable, e.g. \bar{A} or A'
 - Unary operator, i.e. operates on a single variable
 - Also referred to as COMPLEMENT operator





Binary Logic and Basic Gates

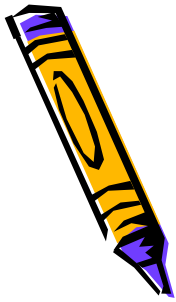

- Digital Circuits and Systems are complex
- However, the basic building blocks of all digital circuits and systems are logic gates
- Logic gates are therefore called the basic primitives of digital systems
- Logic gates in reality are implemented using electronic components such as transistors
- However, we are not concerned with their internal electronic properties but rather their external logic behavior







Standard Symbols




AND

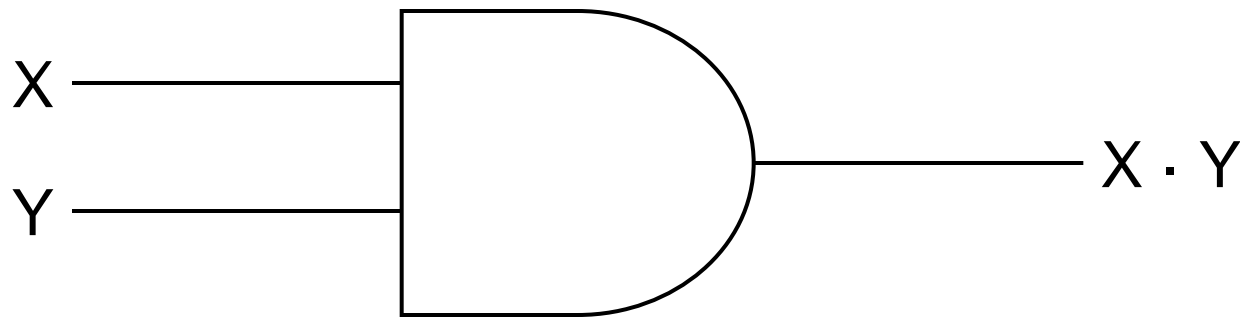

OR

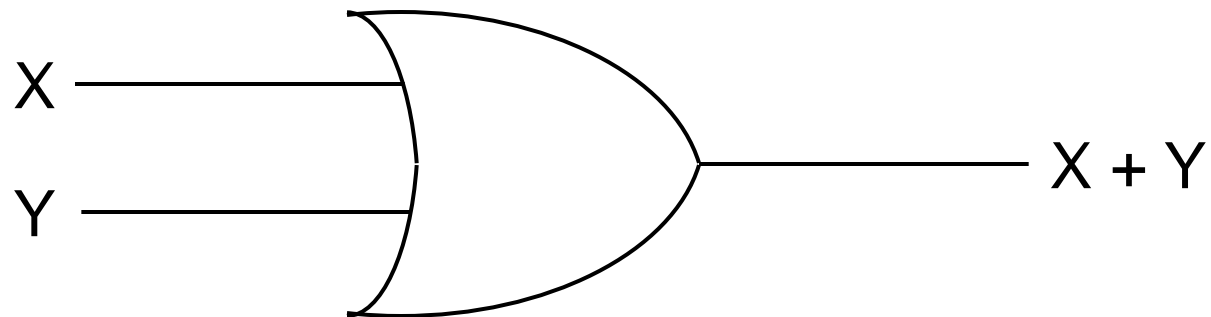

NOT

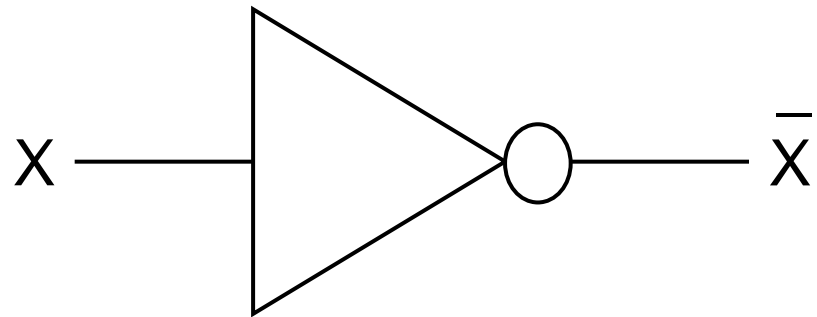



Truth Table



- A table of combinations of the binary variables showing the relationship between the values the variables take on and the values of the result of the operation

AND

X	Y	$Z = X \cdot Y$
0	0	0
0	1	0
1	0	0
1	1	1

OR

X	Y	$Z = X + Y$
0	0	0
0	1	1
1	0	1
1	1	1


NOT

X	$Z = \overline{X}$
0	1
1	0






Gates with More Than Two Inputs

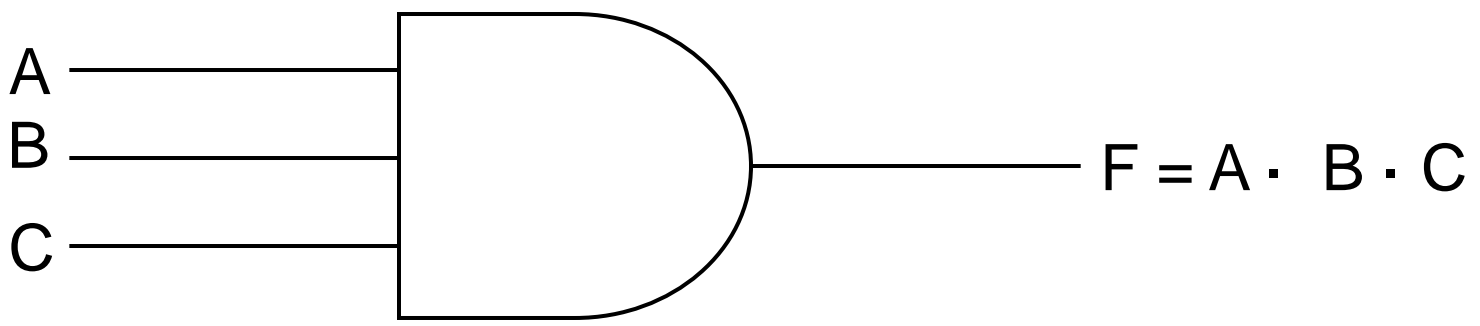

3-Input AND gate

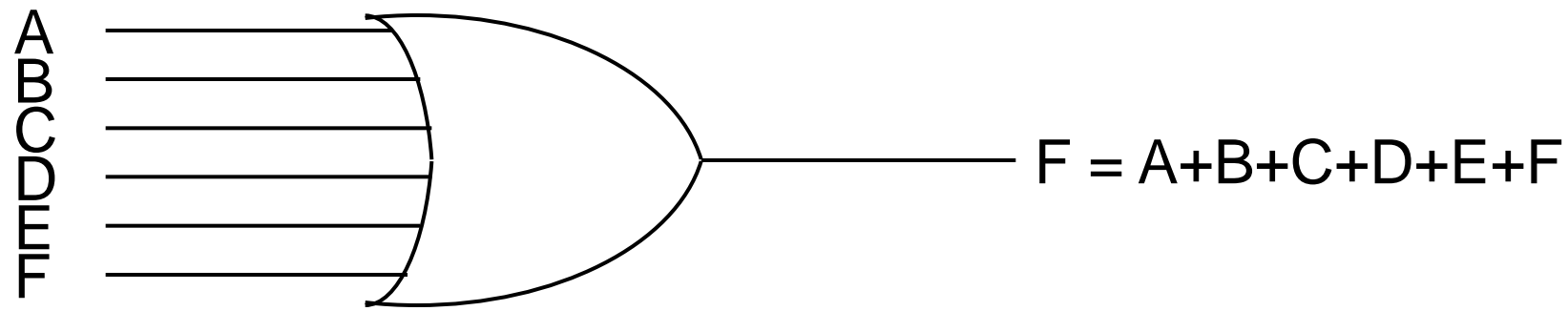

6-Input OR gate





Truth Table



AND			
X	Y	Z	$F = X \cdot Y \cdot Z$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1





Boolean Algebra



- Defines rules of operations on Binary Logic and Logic Functions
- Sometimes similar to Binary Arithmetic but some times different - because binary logic variables can only take on two possible values 0 and 1
- A Boolean function consists of a binary variable denoting the function, an equals sign, and an algebraic expression formed by using binary variables. For example

$$F = X + Y'Z$$





Truth Tables for Boolean Functions



- Truth Table can be constructed for every boolean function
- A boolean function of n -variables will have 2^n rows in its truth table
- These 2^n inputs are formed by counting from 0 to $2^n - 1$
- For example $G(W,X,Y,Z)$ will have 16 rows in the truth table and $F(A,B)$ will have 4 rows





Truth Table for $F = X + Y'Z$




X	Y	Z	Y'	Y'Z	X + Y'Z
0	0	0	1	0	0
0	0	1	1	1	1
0	1	0	0	0	0
0	1	1	0	0	0
1	0	0	1	0	1
1	0	1	1	1	1
1	1	0	0	0	1
1	1	1	0	0	1





Logic Circuit Diagram for $F = X + Y'Z$

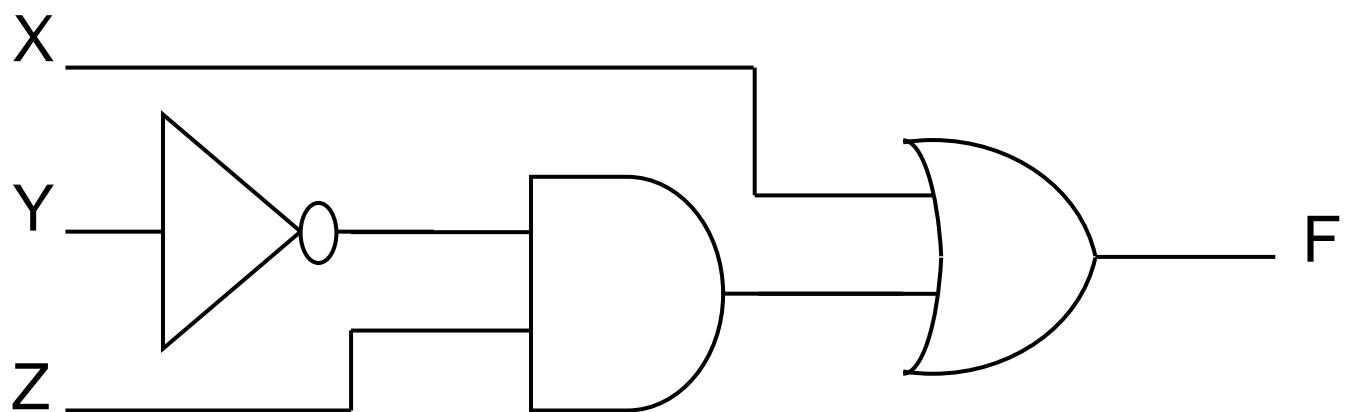





Implementation of a logic circuit using a boolean expression



$$Y = AB(CD' + EF)$$



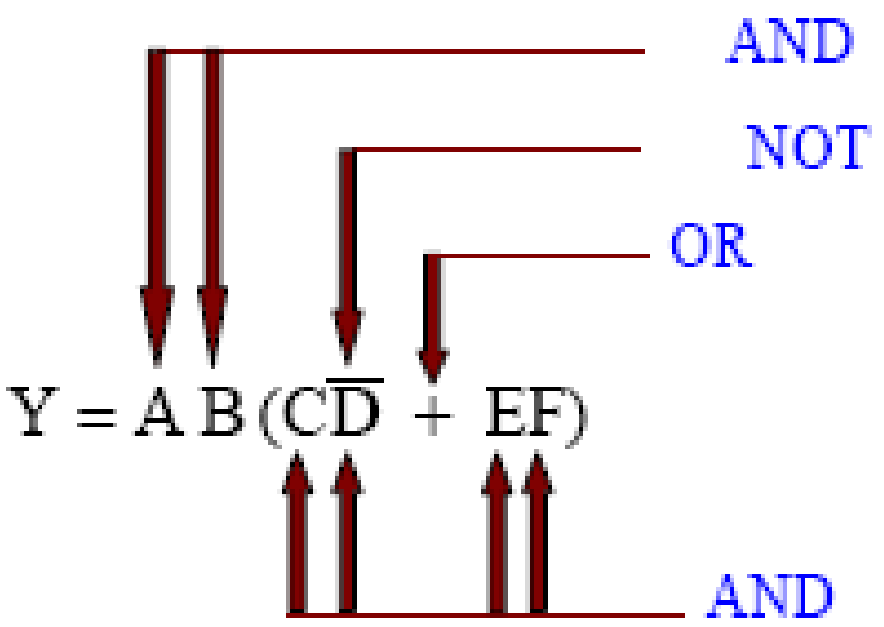




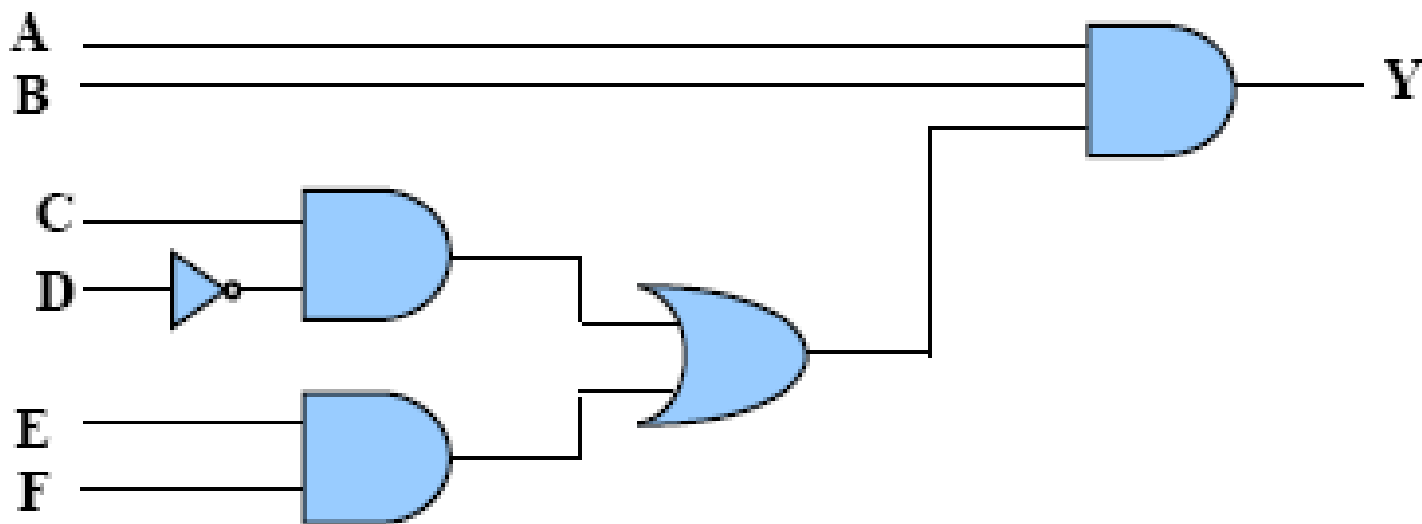


$$Y = AB(CD' + EF)$$





Timing Diagram

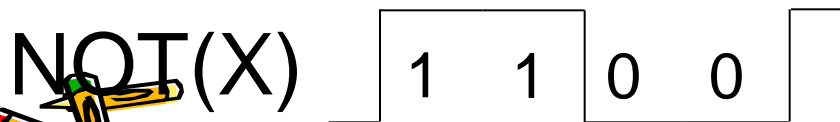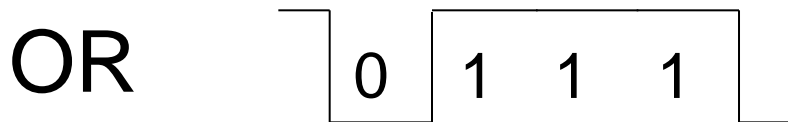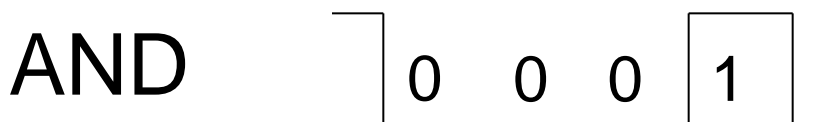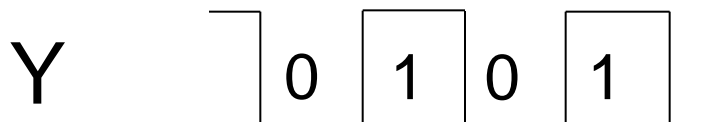

❑ Horizontal axis represents time

❑ Vertical axis shows the value of the signal

❑ High voltage level represents 1 and low voltage level represents 0

❑ Timing diagrams are very important in digital systems design and verification





Basic Identities of Boolean Algebra



1. $X + 0 = X$

2. $X \cdot 1 = X$

3. $X + 1 = 1$

4. $X \cdot 0 = 0$

5. $X + X = X$

6. $X \cdot X = X$

7. $X + X' = 1$

8. $X \cdot X' = 0$

9. $(X')' = X$





Basic Identities of Boolean Algebra



1. $X + Y = Y + X$

2. $XY = YX$

Commutative

3. $X + (Y + Z) = (X + Y) + Z$

4. $X(YZ) = (XY)Z$

Associative

5. $X(Y+Z) = XY + XZ$

6. $X + YZ = (X+Y)(X+Z)$

Distributive

7. $(X + Y)' = X'Y'$

8. $(XY)' = X' + Y'$

DeMorgan's





OR

1	$x+1 = 1$
2	$x+x' = 1$
3	$x+x = x$
4	$x+0 = x$
5	$(x')' = x$
6	$x+y = y+x$
7	$x+(y+z) = (x+y)+z$
8	$x.(y+z) = x.y+x.z$
9	$(x+y)' = x'.y'$
10	$x+(x.y) = x$

AND

1	$x.1 = x$
2	$x.x' = 0$
3	$x.x = x$
4	$x.0 = 0$
5	$(x')' = x$
6	$x.y = y.x$
7	$x.(y.z) = (x.y).z$
8	$x+y.z = (x+y).(x+z)$
9	$(x.y)' = x'+y'$
10	$x.(x+y) = x$





Algebraic Manipulation




- Using basic identities a boolean function can be simplified
- For example

$$F = X'YZ + X'YZ' + XZ$$





Algebraic Manipulation

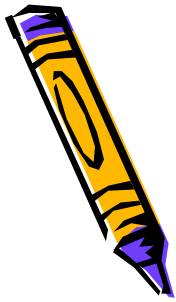

- Using basic identities a boolean function can be simplified
- For example

$$\begin{aligned} F &= X'YZ + X'YZ' + XZ \\ &= X'Y(Z + Z') + XZ \\ &= X'Y \cdot 1 + XZ \\ &= X'Y + XZ \end{aligned}$$





Algebraic Manipulation Examples



1. $X + XY =$

2. $XY + XY' =$

3. $X + X'Y =$

4. $X(X + Y) =$

5. $(X + Y)(X + Y') =$

6. $X(X' + Y) =$





Algebraic Manipulation Examples



1. $X + XY = X(1+Y) = X$





Algebraic Manipulation Examples



$$2. XY + XY' = X(Y + Y') = X$$





Algebraic Manipulation Examples



$$3. X + X'Y = (X + X')(X + Y) = X + Y$$





Algebraic Manipulation Examples



$$4 . X (X + Y) = X + XY = X (1 + Y) = X$$





Algebraic Manipulation Examples



1. $X + XY = X (1+Y) = X$
2. $XY + XY' = X (Y + Y') = X$
3. $X + X'Y = (X + X') (X + Y) = X + Y$
4. $X (X + Y) = X + XY = X (1 + Y) = X$
5. $(X + Y)(X + Y') = X + XY' + XY + YY'$
 $= X (1 + Y') + XY$
 $= X \cdot X + XY$
 $= X + XY$
 $= X (1 + Y)$
 $= X$
6. $X(X' + Y) = XX' + XY = XY$





Algebraic Manipulation Examples



$$\begin{aligned} 5. (X + Y)(X + Y') &= X + XY' + XY + YY' \\ &= X(1 + Y') + XY \\ &= X \cdot 1 + XY \\ &= X + XY \\ &= X(1 + Y) \\ &= X \end{aligned}$$





Algebraic Manipulation Examples



$$6 . X(X' + Y) = \textcolor{red}{XX'} + \textcolor{red}{XY} = \textcolor{red}{XY}$$





Algebraic Manipulation Examples



1. $X + XY = X(1+Y) = X$
2. $XY + XY' = X(Y + Y') = X$
3. $X + X'Y = (X + X')(X + Y) = X + Y$
4. $X(X + Y) = X + XY = X(1 + Y) = X$
5. $(X + Y)(X + Y') = X + XY' + XY + YY'$
 $= X(1 + Y') + XY$
 $= X \cdot 1 + XY$
 $= X + XY$
 $= X(1 + Y)$
 $= X$
6. $X(X' + Y) = XX' + XY = XY$





Example

- Simplify the following Boolean expression and implement logic circuit for it



$$Y = A'B'C' + A'B'C + A'BC + ABC$$




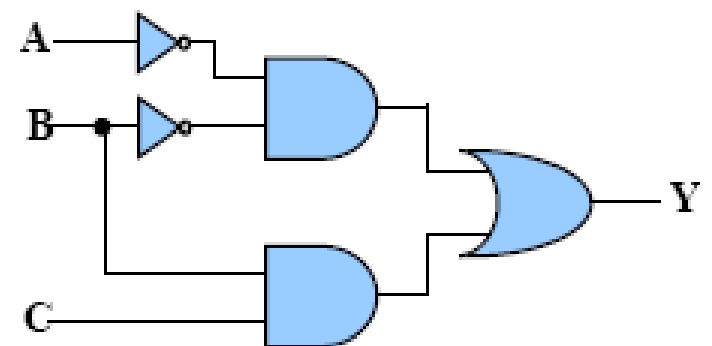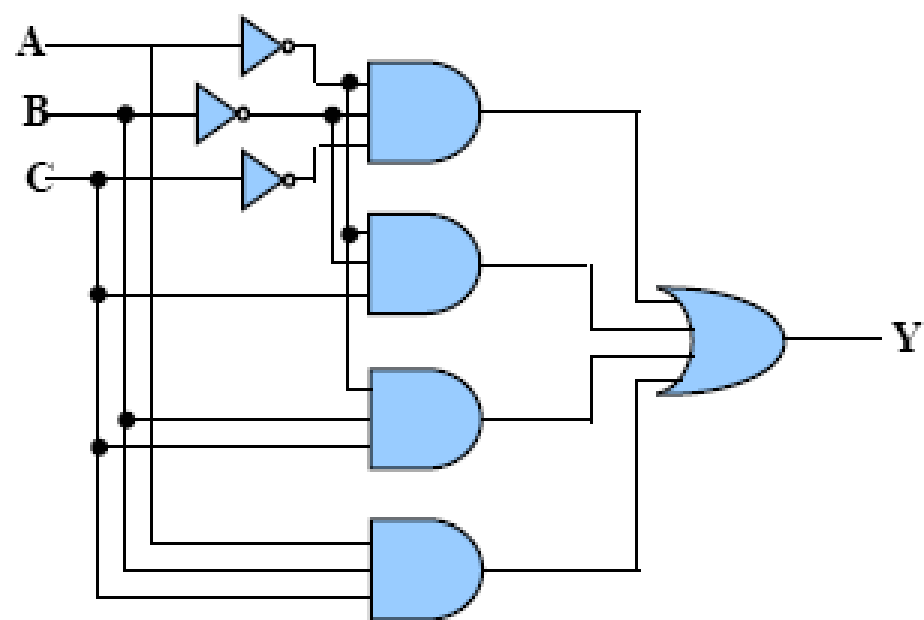
$$\begin{aligned} Y &= A'B'C' + A'B'C + A'BC + ABC \\ &= A'B'(C' + C) + BC(A' + A) \\ &= A'B' + BC \end{aligned}$$







Combinational logic circuits





NOR & NAND





Basic Identities of Boolean Algebra



1. $X + Y = Y + X$

2. $XY = YX$

Commutative

3. $X + (Y + Z) = (X + Y) + Z$

4. $X(YZ) = (XY)Z$

Associative

5. $X(Y+Z) = XY + XZ$

6. $X + YZ = (X+Y)(X+Z)$

Distributive

7. $(X + Y)' = X'Y'$

8. $(XY)' = X' + Y'$

DeMorgan's





$$(A + B)' = A'B'$$

$$(AB)' = A' + B'$$

$$\overline{A + B} = \overline{A} \bullet \overline{B}$$

$$\overline{A \bullet B} = \overline{A} + \overline{B}$$

نظرية دي مورجان الأولى:

نظرية دي مورجان الثانية:






$$\overline{A \bullet B} = \overline{A} + \overline{B}$$

NAND

Negative-OR

Example

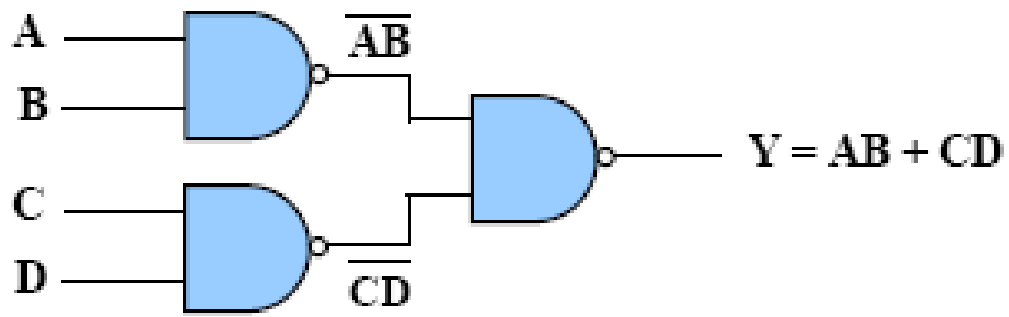

$$Y = \overline{\overline{AB}} \overline{\overline{CD}}$$

From Demorgan Theorem

$$Y = \overline{\overline{AB}} + \overline{\overline{CD}}$$


$$\text{Then } Y = AB + CD$$





$$\overline{A + B} = \overline{A} \bullet \overline{B}$$

NOR ↑ ↑ Negative-AND

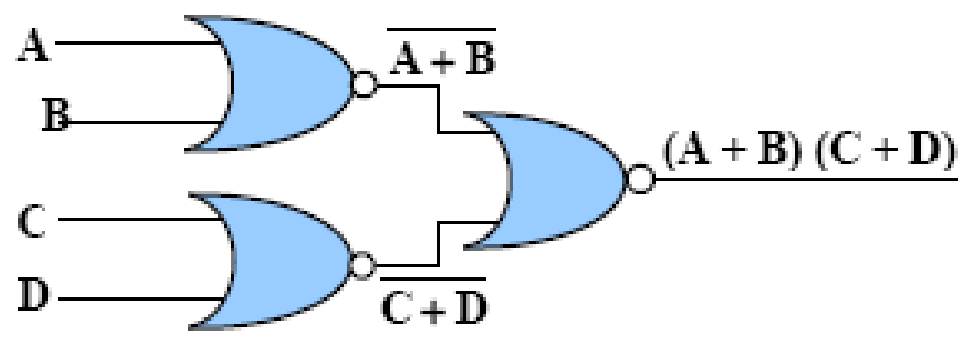

$$Y = \overline{\overline{A + B} + \overline{C + D}}$$

From Demorgan Theorem

$$Y = \overline{\overline{A + B}} \bullet \overline{\overline{C + D}}$$

$$Y = (A + B) \bullet (C + D)$$





طبق نظريات ديمورجان على التعبير البولياني التالي:



$$Y = \overline{(A + \overline{B} + \overline{C}) \bullet (\overline{A} + B + \overline{C})}$$





$$\begin{aligned} Y &= \overline{(A + \bar{B} + \bar{C})} \bullet \overline{(\bar{A} + B + \bar{C})} \\ &= \overline{(A + \bar{B} + \bar{C})} + \overline{(\bar{A} + B + \bar{C})} \\ &= \bar{A} \bar{\bar{B}} \bar{\bar{C}} + \bar{\bar{A}} \bar{B} \bar{\bar{C}} = \bar{A} B C + A \bar{B} C \end{aligned}$$





طبق نظريات ديهورجان على التعبير البولييني التالي:

$$Y = \overline{(\overline{A} + B) + CD}$$





$$\begin{aligned} Y &= \overline{(\overline{\overline{A}} + \overline{B}) + CD} \\ &= \overline{(\overline{A} + B). \overline{CD}} \\ &= (\overline{\overline{A}}. \overline{\overline{B}})(\overline{\overline{C}} + \overline{\overline{D}}) \\ &= A\overline{B}(\overline{C} + \overline{D}) \end{aligned}$$







Thank you





H

A

K

T

W

P





H

A

K

T

B

P



