



Logical Design


CS 221

Prof.Dr. Mohamed Osama Khozium





Combinational logic circuits

 



NOR & NAND
XOR & XNOR
Half & Full Adder
Decoder
Multiplexer






$$\overline{A \bullet B} = \overline{A} + \overline{B}$$

NAND

Negative-OR

Example

 

$$Y = \overline{\overline{AB}} \overline{\overline{CD}}$$

From Demorgan Theorem

$$Y = \overline{\overline{AB}} + \overline{\overline{CD}}$$


$$\text{Then } Y = AB + CD$$





$$\overline{A + B} = \overline{A} \bullet \overline{B}$$

NOR   Negative-AND

 

$$Y = \overline{\overline{A + B} + \overline{C + D}}$$

From Demorgan Theorem

$$Y = \overline{\overline{A + B}} \bullet \overline{\overline{C + D}}$$

$$Y = (A + B) \bullet (C + D)$$






Exclusive-OR Gate XOR-gate

IN		OUT	
A	B	Y	
0	0	0	$A'B'$
0	1	1	$A'B$
1	0	1	AB'
1	1	0	AB

$$Y = \overline{A}B + A\overline{B}$$


$$Y = A \oplus B$$

 



$$Y = \overline{A}B + A\overline{B}$$

$$Y = A \oplus B$$


 


XOR represented by AND & OR & NOT





Timing Diagram

  

$$Y = A \oplus B$$







Exclusive-NOR Gate XNOR-gate

IN		OUT	
A	B	Y	
0	0	1	$A'B'$
0	1	0	$A'B$
1	0	0	AB'
1	1	1	AB

$$Y = AB + \overline{AB}$$



$$Y = A \odot B$$

 

 

XNOR represented by AND & OR & NOT



  



Half Adder





Half Adder

Follow The Design Procedures

(1) Determine inputs : A & B
Determine outputs : S & C

(2) Derive the truth table :

A	B		S	C
0	0		0	0
0	1		1	0
1	0		1	0
1	1		0	1

(3) Obtain the simplified Boolean functions :

$$S = A' B + A B' = A \oplus B$$



$$C = A B$$






(4)

Draw the logic diagram :

  

(5)

Verify the correctness of the design :

 



Full Adder

(1) Inputs : A, B Cin

Output : S, C

(2)

A	B	Cin		S	C
0	0	0		0	0
0	0	1		1	0
0	1	0		1	0
0	1	1		0	1
1	0	0		1	0
1	0	1		0	1
1	1	0		0	1
1	1	1		1	1

(3)

$$S = A' B' Cin + A' B Cin' + A B' Cin' + A B Cin$$

$$C = A' B Cin + A B' Cin + A B Cin' + A B Cin$$





(3) $S = A' B' C_{in} + A' B C_{in}' + A B' C_{in}' + A B C_{in}$

$$C = A' B C_{in} + A B' C_{in} + A B C_{in}' + A B C_{in}$$

$$S = (A' B + A B') C_{in}' + (A' B' + A B) C_{in}$$


$$= (A \oplus B) C_{in}' + (A \odot B) C_{in}$$

$$= (A \oplus B) C_{in}' + \overline{(A \oplus B)} C_{in}$$

$$= A \oplus B \oplus C_{in}$$


$$C_{in} = Y ; A \oplus B = X$$

 
$$\therefore S = XY' + X'Y \Rightarrow S = X \oplus Y$$




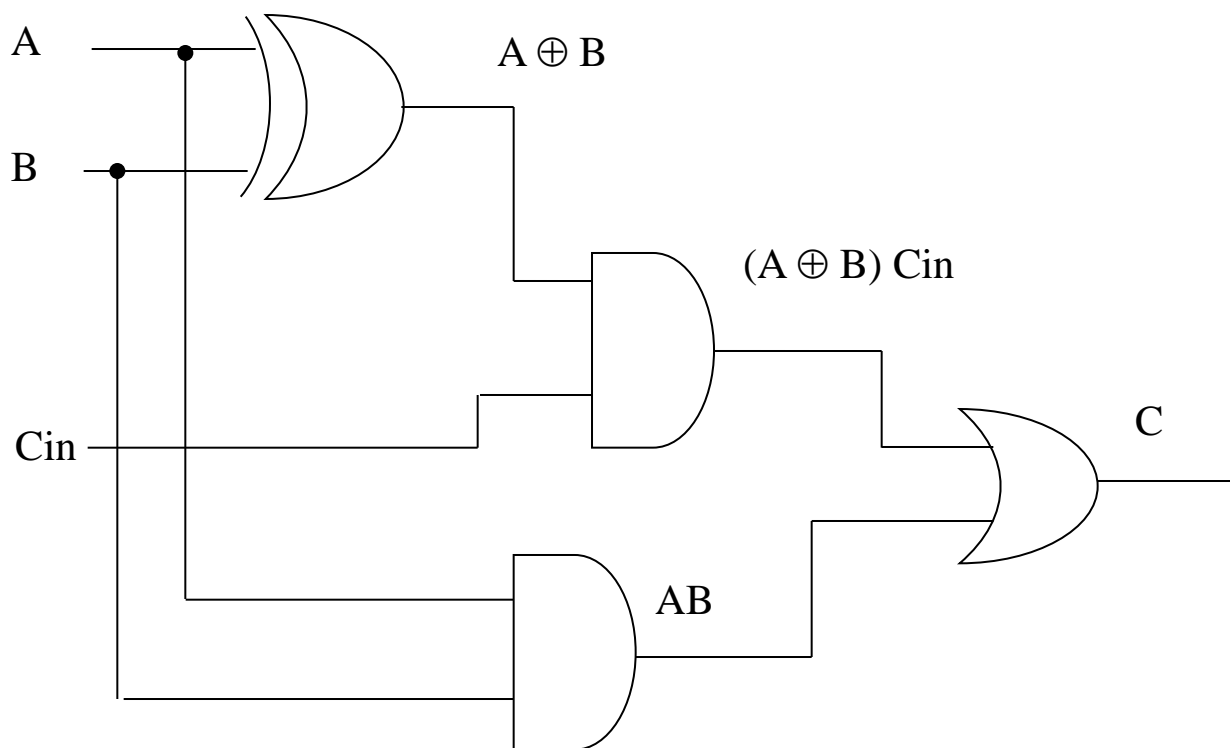
$$C = AB (C_{in} + C_{in}') + C_{in} (A'B + AB')$$
$$= AB + C_{in} (A \oplus B)$$



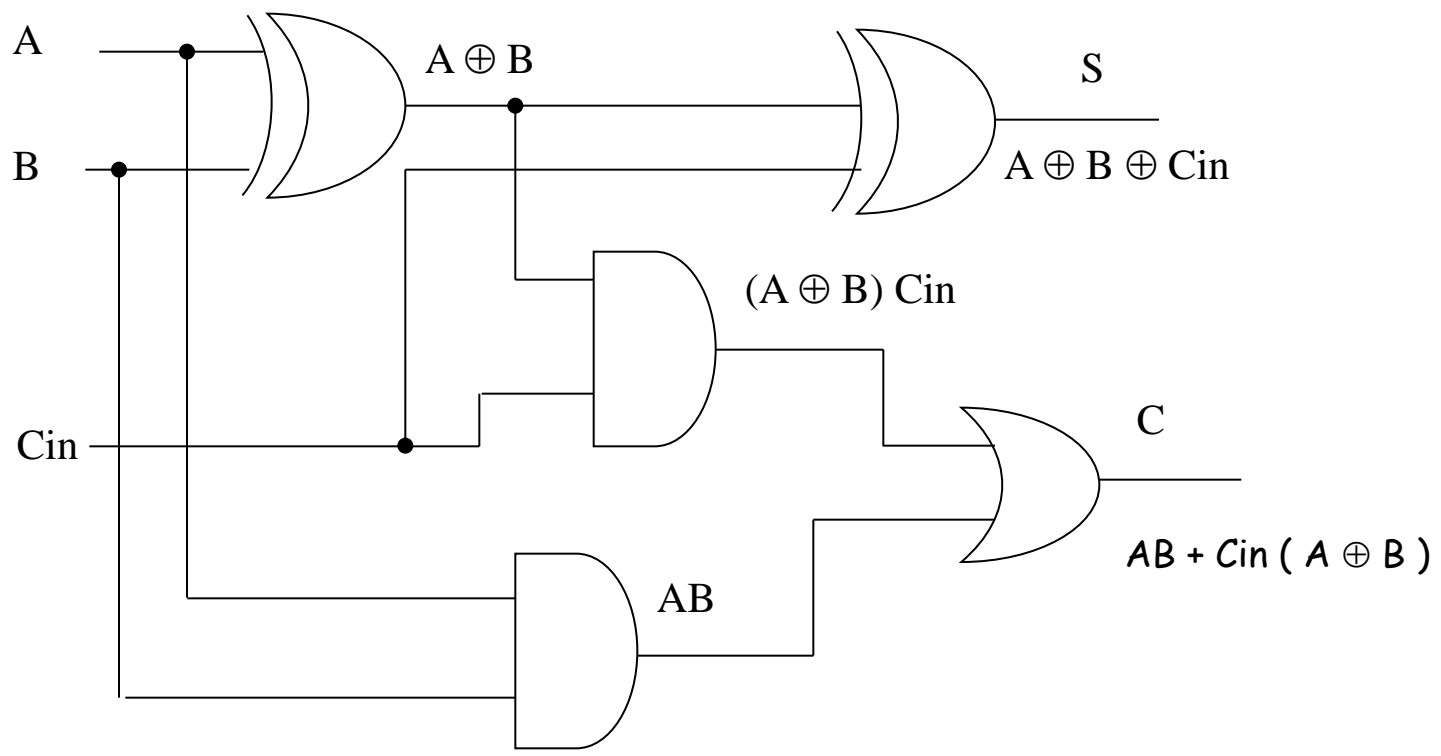




Decoders



Decoders are important type of combinational circuit. Address decoders with n inputs can select any of 2^n locations.

 They are useful in selecting a memory location according a binary value place don the address lines of a memory bas.



Block diagram for a decoder








Decoder 2*4

Inputs			Outputs			
	A	B	D3	D2	D1	D0
0	0	0	0	0	0	1
1	0	1	0	0	1	0
2	1	0	0	1	0	0
3	1	1	1	0	0	0

Inputs = 2

Outputs = 4

 

  


Decoder Block Diagram 2×4






Decoder 3*8

 

Decoder 4*16

 



Decoder with enable

Decoder works when enable = 1

Decoder doesn't work when enable = 0





Inputs			Outputs			
E	A	B	D3	D2	D1	D0
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

Inputs			Outputs			
E	A	B	D3	D2	D1	D0
0	×	×	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0






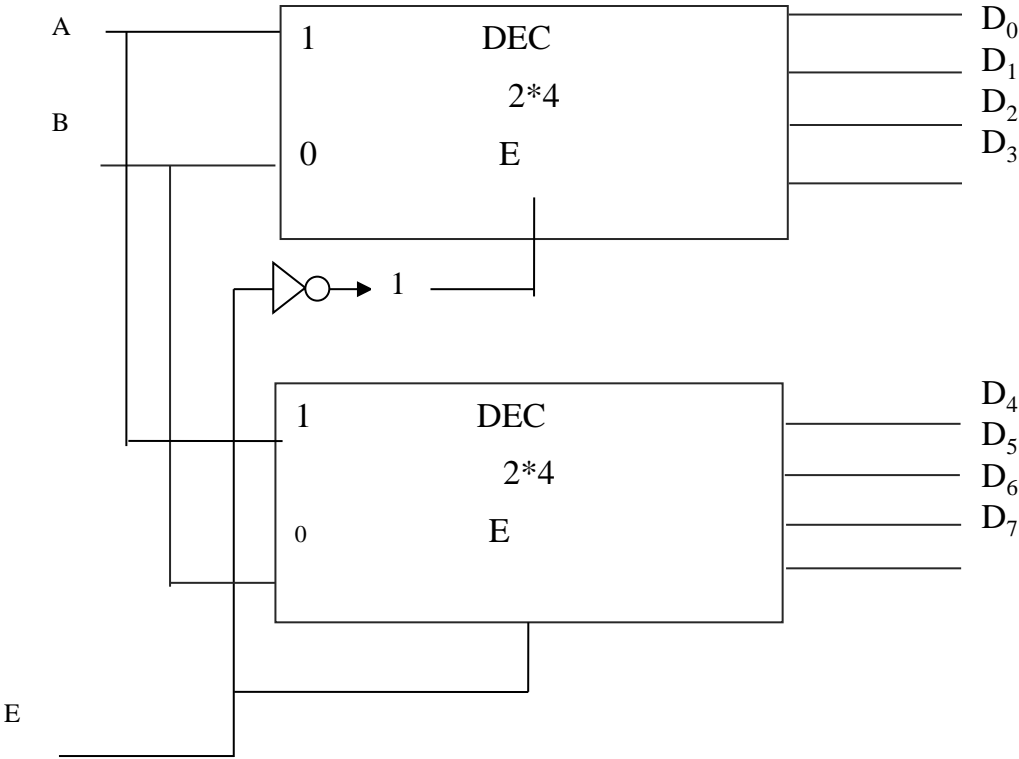 Designing 3*8 Decoder using 2*4 decoder and enable.





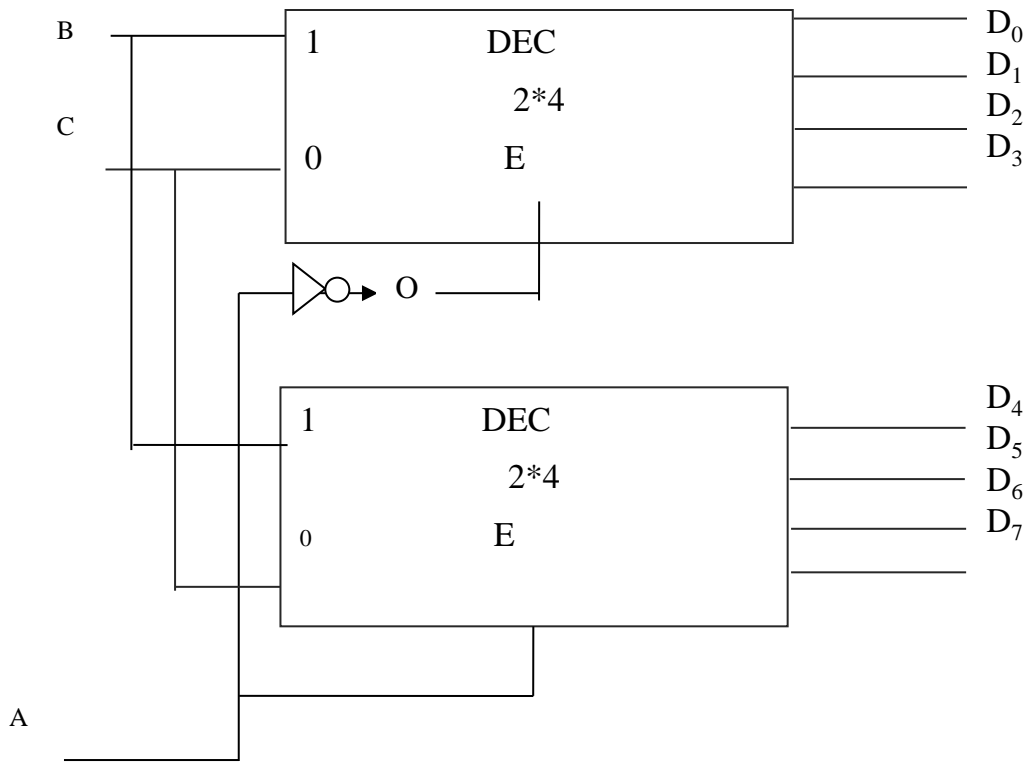Designing 3*8 Decoder using 2*4 decoder and enable.





Multiplexer

A multiplexer has 2^n inputs, 1 outputs and n selections

$$N = 3$$

= 8 ... المدخلات $\Rightarrow 2^n$

= 1 المخرجات

= 3 الاختيارات

Multiplexer 2*1

2 inputs

1 outputs

1 selection

selection	Inputs		Outputs
S	X	Y	Q
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

إذا كانت قيم $S = 0$ فإن قيم المزج Q هي قيم Y


إذا كانت قيم $S = 1$ فإن قيم المزج Q هي قيم X






		X	
		1	1
S	0	1	3
	4	5	1
		Y	
		7	6

$$Q = Y S' + X S$$

 


Block D

 



Multiplexer


4×1

 



 Example :

Implement the following function $F(X,Y,Z) = \sum (3,5,6)$ using an 8×1 Multiplexer







Thank you

