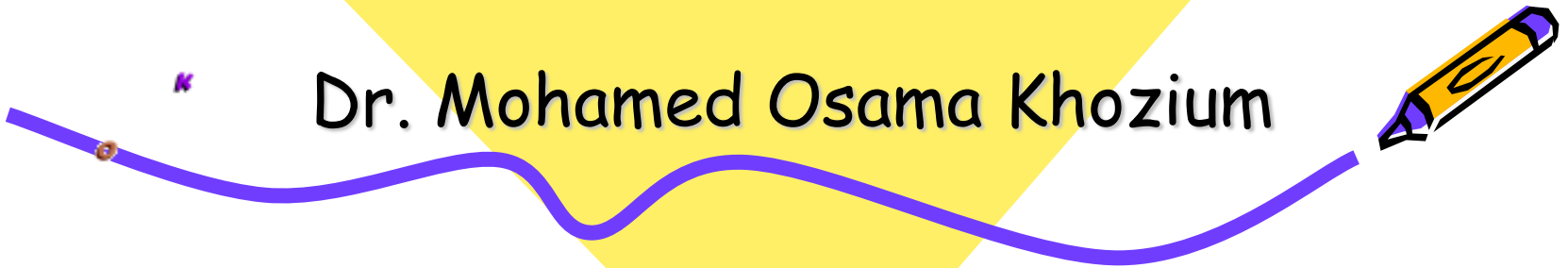





Logic Design


CSE 221

Dr. Mohamed Osama Khozium



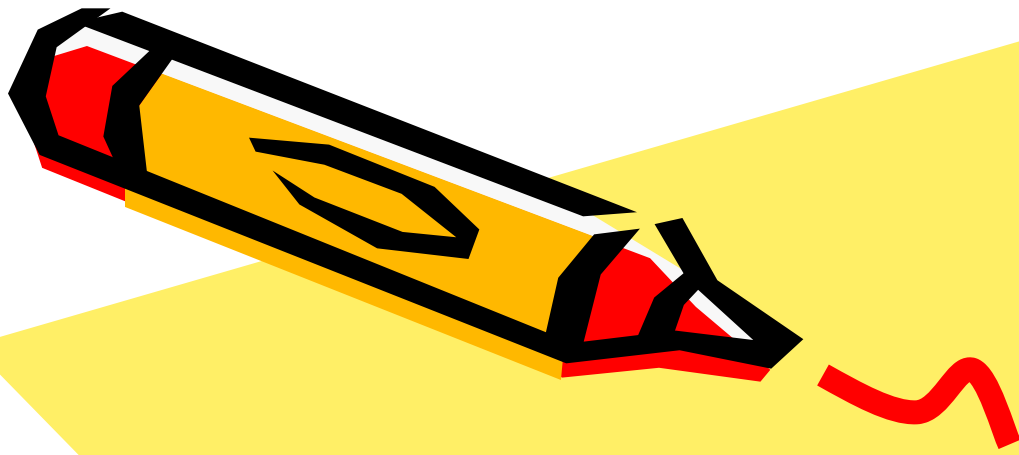

Design Procedure

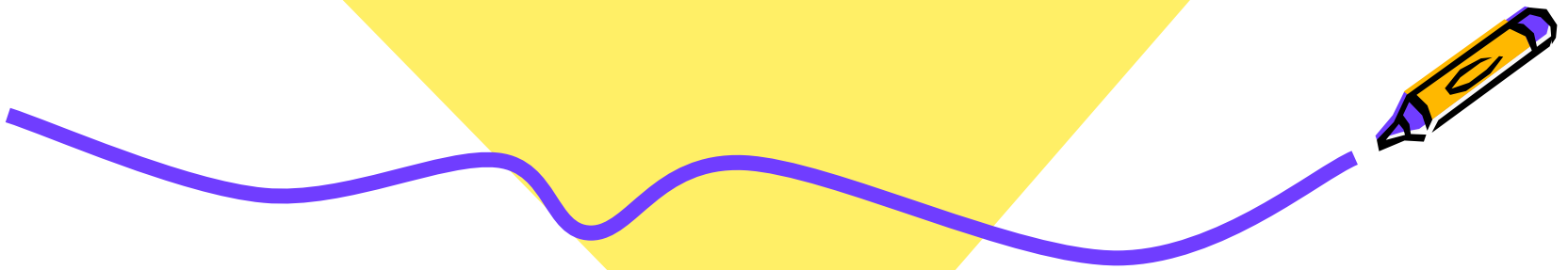



Design Procedure



1. From the specifications of the circuit, determine the required number of inputs and outputs and assigned a letter symbol to each
2. Derive the truth table that defined the relationship between inputs and outputs
3. Obtain the simplified Boolean functions for each output as a function of the input variables
4. Draw the logic diagram
5. Verify the correctness of the design






Some Design Examples



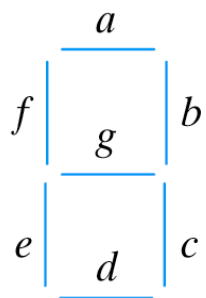- BCD to Excess-3 code converter
- BCD to Seven Segment Decoder



(a) Segment designation



(b) Numerical designation for display

Fig. P4-9





BCD to Excess-3 code converter



□ **TABLE 3-2**

Truth Table for Code Converter Example


Decimal Digit	Input BCD				Output Excess-3			
	A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0

▷ 9 (in) → X (don't care) in output till 15





InPuts				OutPuts			
A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	x	x	x	x
1	0	1	1	x	x	x	x
1	1	0	0	x	x	x	x
1	1	0	1	x	x	x	x
1	1	1	0	x	x	x	x
1	1	1	1	x	x	x	x

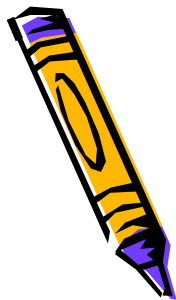



BCD to Excess-3 code converter K- Maps




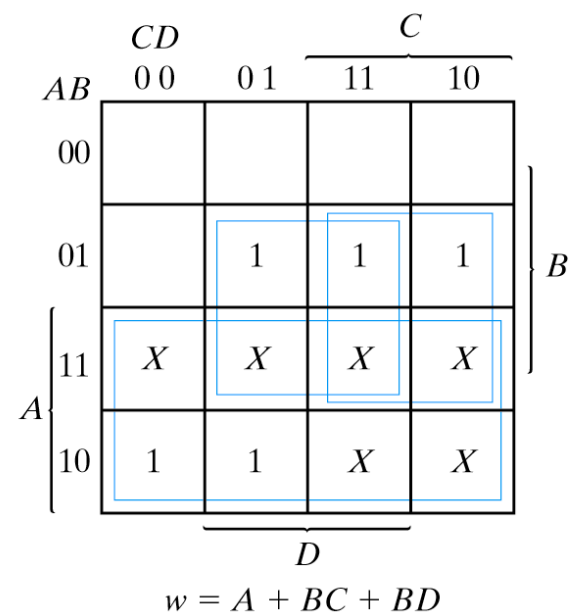
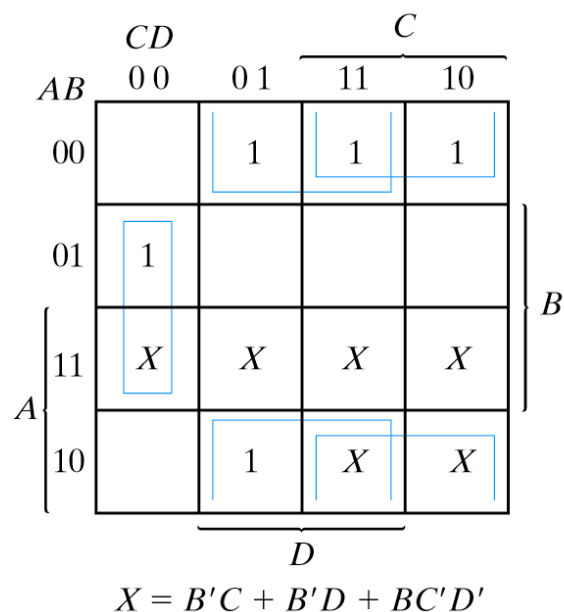


Fig. 4-3 Maps for BCD to Excess-3 Code Converter

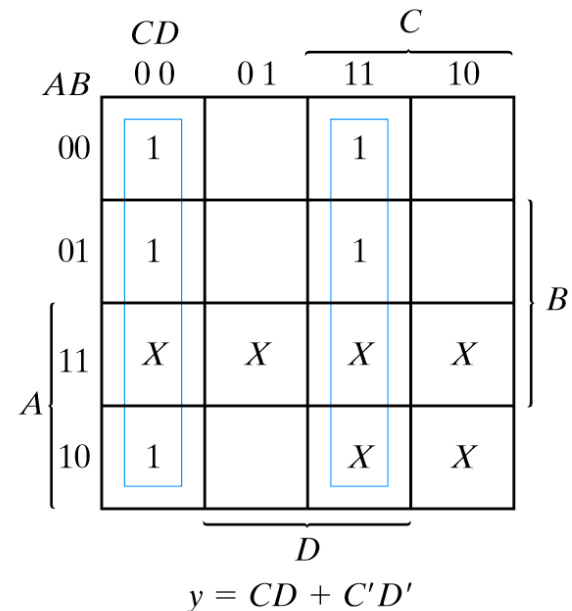

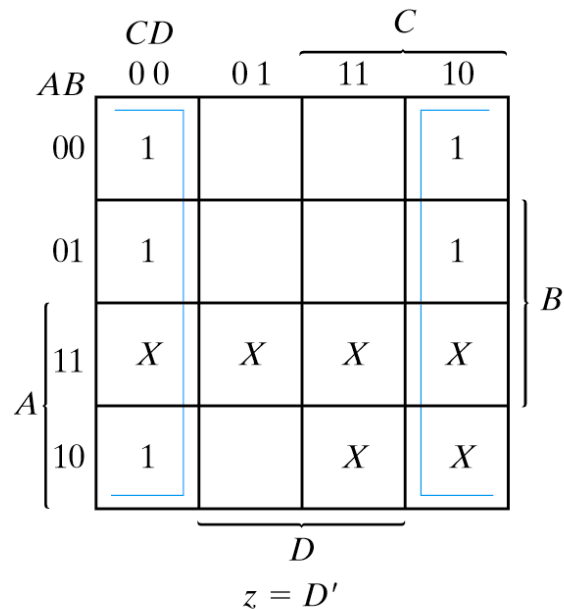

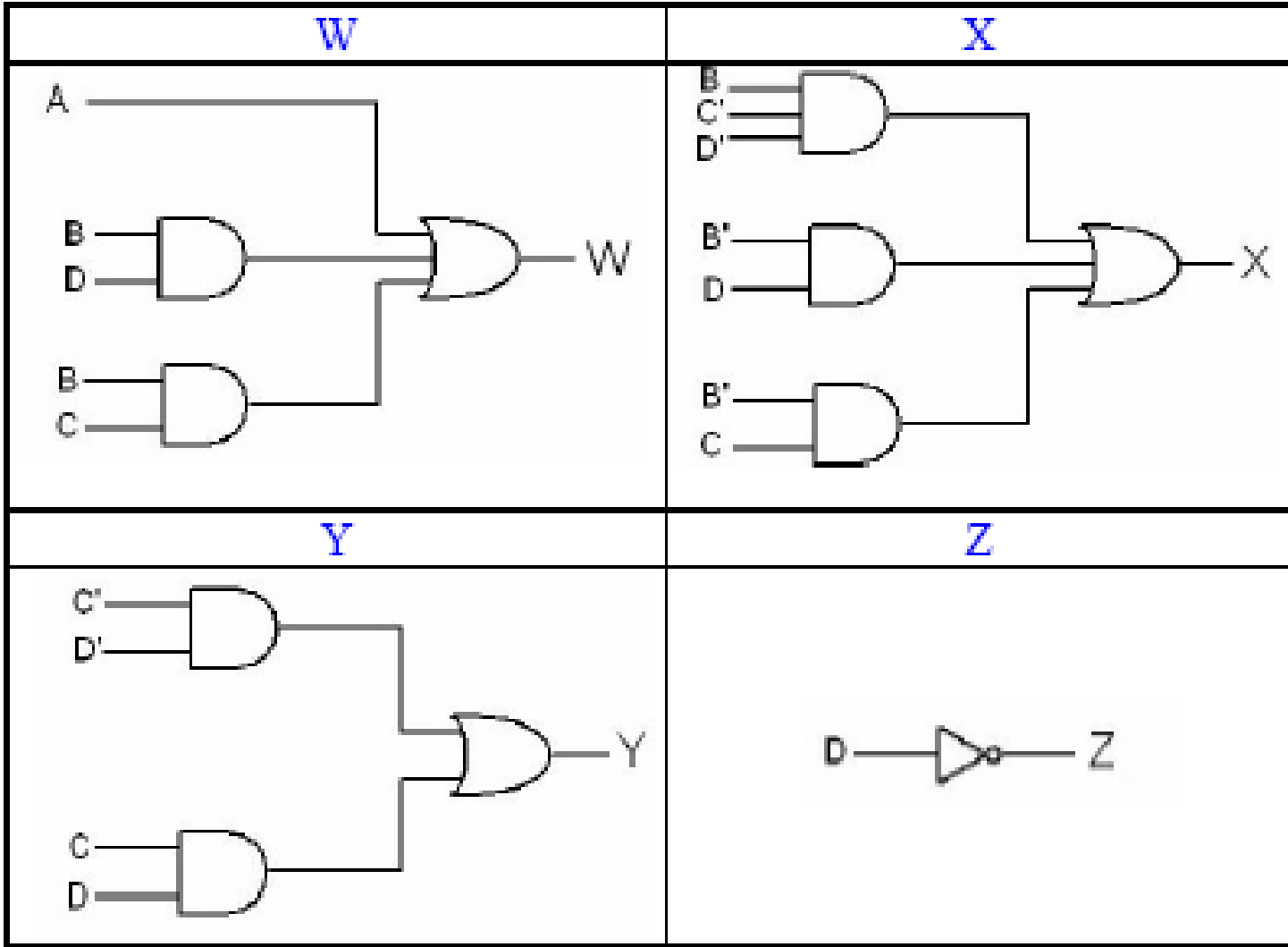

BCD to Excess-3 code converter

Logic Diagram

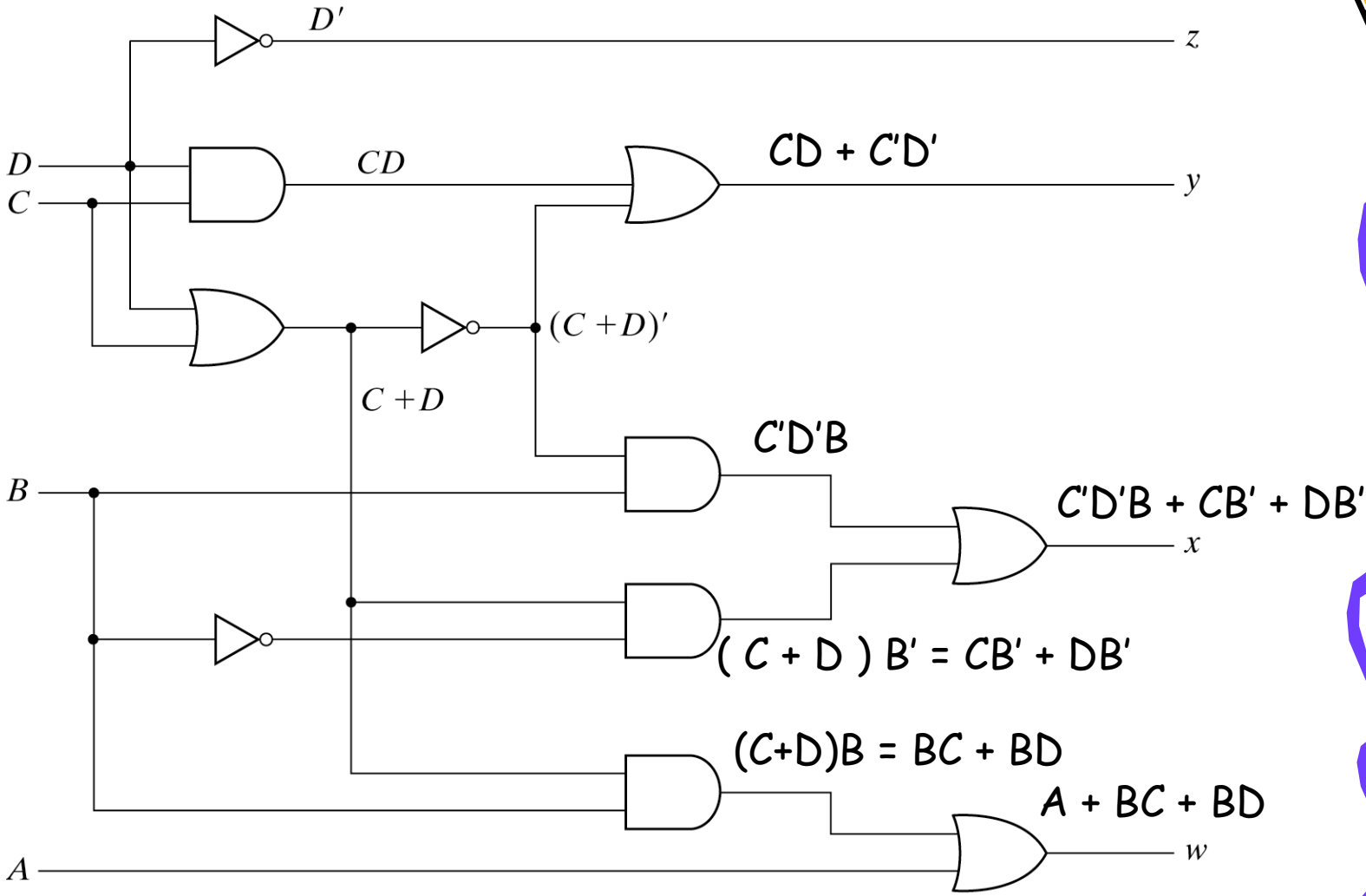


Fig. 4-4 Logic Diagram for BCD to Excess-3 Code Converter







Thank you



